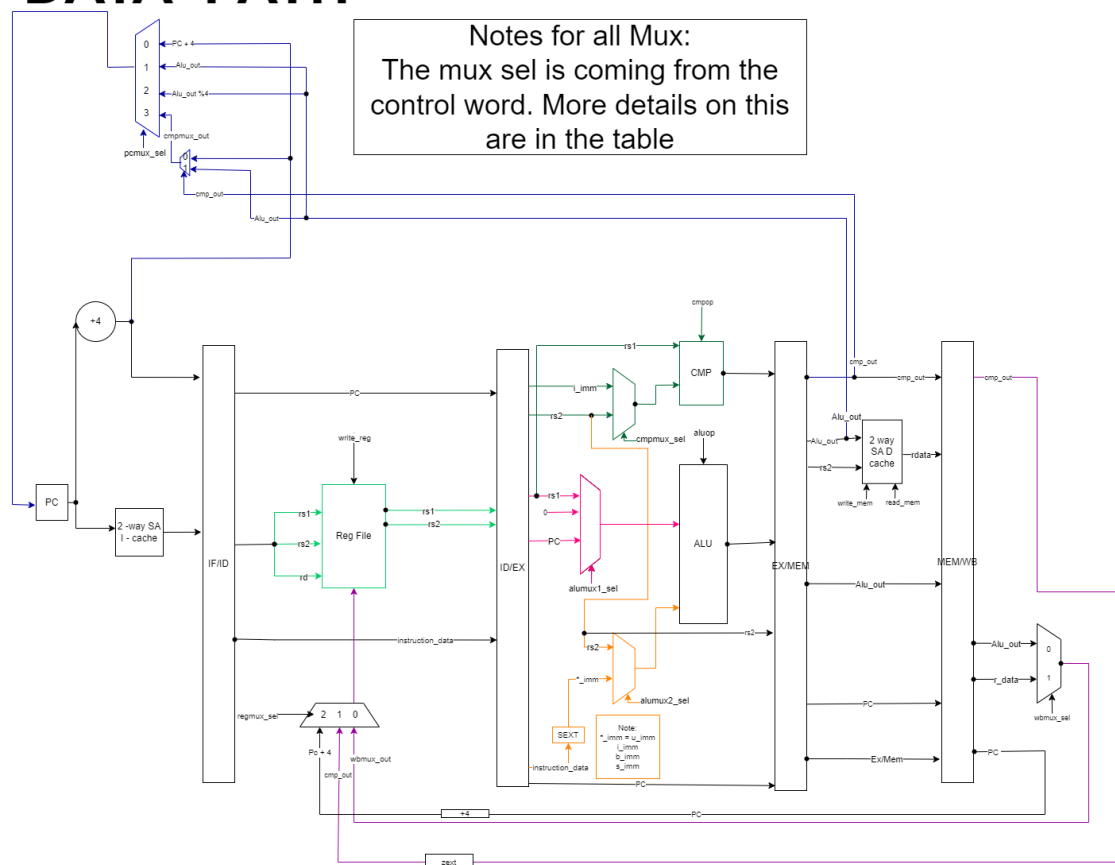


ECE 411 MP 4 Basic Datapath Design


Introduction:

For this MP, we are developing a pipelined processor using the knowledge we have gained from the course lectures. Aside from the basic datapath and handling the standard CPU instructions, we will implement forwarding and branch prediction to help improve performance. The design for the Hazard Detection Unit and Forwarding Unit has not been done. We hope to complete that in parallel with our checkpoint 1. We will continue to increase performance in future checkpoints by having L1 (2-way SA) and L2 (8-way SA). We have yet to decide other advanced features, but we hope to decide on that after we build our pipelined CPU.

Datapath:



Memory Block unit

 

bit 23

Control Word (23:0)
 Control Word is generated by the opcode of the instruction and passed down the pipeline.
 Signals are grouped by the stage that they are used in, not necessarily the stage that contains their units

Bit 0

Note:

func3 will be filled in with the appropriate value for each instruction type, it is noted as func3 instead of constant value to shorten table.

mem_byt_en will be filled with appropriate value for each instruction type, it is noted as a range 0000-

Instruction	IF	ID	EX	MEM			WB		
	pcmux_sel[1:0]		cmpop[2:0] cmpmux_sel	aluop[2:0] alumux1_sel[1:0] alumux2_sel[2:0]	read_mem	write_mem	mem_byt_en[3:0]	wbmux_sel write_reg regmux_sel[1:0]	
ldr	pc+4		x x add rs1_out s_imm	1	0	xxxx	rdata	1	wbmux_out
str	pc+4		x x add rs1_out s_imm	0	1	0000-1111	x	0	x
imm rest (x8)	pc+4		x x funct3 rs1_out i_imm	0	0	xxxx	alu_out	1	wbmux_out
slt	pc+4		bit i_imm funct3 rs1_out i_imm	0	0	x	x	1	cmp_out
sltu	pc+4		bitu i_imm funct3 rs1_out i_imm	0	0	x	x	1	cmp_out
sra	pc+4		x x sra rs1_out i_imm	0	0	x	alu_out	1	wbmux_out
sr	pc+4		x x srl rs1_out i_imm	0	0	x	alu_out	1	wbmux_out
reg rest	pc+4		x x funct3 rs1_out rs2_out	0	0	x	alu_out	1	wbmux_out
add	pc+4		x x add rs1_out rs2_out	0	0	x	alu_out	1	wbmux_out
sub	pc+4		x x sub rs1_out rs2_out	0	0	x	alu_out	1	wbmux_out
slt	pc+4		bit rs2_out funct3 rs1_out rs2_out	0	0	x	x	1	cmp_out
slt_u	pc+4		bitu rs2_out funct3 rs1_out rs2_out	0	0	x	x	1	cmp_out
sra	pc+4		x x sra rs1_out rs2_out	0	0	x	alu_out	1	wbmux_out

sr	pc+4	x	x	srl	rs1_out	rs2_out	0	0	x	alu_out
jalr	alu_mod2	x	x	add	rs1_out	i_imm	0	0	x	x
jal	alu_out	x	x	add	pc_out	j_imm	0	0	x	x
br	cmpmux_out	fucnt3	funct3	add	pc_out	b_imm	0	0	xxxx	x
lui	pc+4	x	x	add	0	u_imm	0	0	x	alu_out
auipc	pc+4	x	x	add	pc_out	u_imm	0	0	x	alu_out